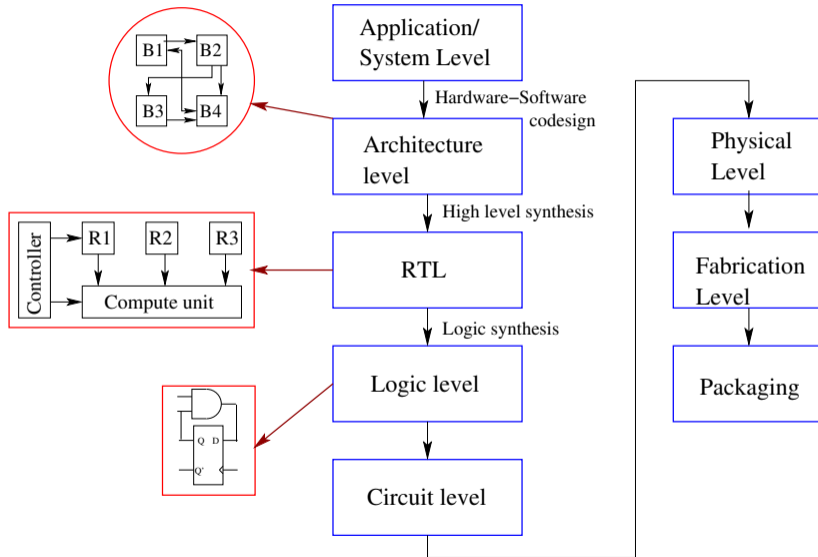


# Verilog: Hardware Description Language



Arijit Mondal  
Dept. of CSE

# Digital CAD flow




# Introduction

- Verilog was designed primarily for digital hardware designers developing FPGAs and ASICs.
- It is different from C/C++/Java.
- Uses discrete event simulation techniques
- This is one of the most commonly used languages for describing hardware. Other popular language is VHDL
- Supports both structural as well as behavioral description

# Structural vs Behavioral

- Structural

- \* Connectivities of gates

 

- Behavioral

- \* Behavior of module

- \*  $out = SA + \bar{S}B$

# Concept of module


- Basic unit is module that describes a hardware component
  - \* Modules cannot contain definitions of other modules.
  - \* A module can, however, be instantiated within another module.
  - \* Allows the creation of a hierarchy in a Verilog description.

# Syntax of module definition

```
module module_name(list_of_ports);  
    input /output declaration;  
    local net declaration;  
    statements;  
endmodule
```
 
# MUX : Structural form

```
module MUX(out, A, B, S);  
    output out;  
    input A, B, S;  
    wire I1, I2, I3;  
  
    and G1(I2, A, S);  
    and G3(I3, I1, B);  
    not G2(I1, S);  
    or G4(out, I2, I3);  
  
endmodule
```




# Primitive gates

- and, or, nand, not, nor, xor, xnor, buf
- Syntax: `<gate_name> <inst_name> (<out>,<in1>,<in2>);`
- Syntax: `<gate_name> <inst_name> (<out>,<in1>);`


 
# Hierarchical design

```
module mux4x1(y,i1,i2,i3,i4,s0,s1);  
input i1,i2,i3,i4,s0,s1;  
output y;  
  
MUX MUX_01(y01,i1,i2,s0);  
MUX MUX_02(y02,i3,i4,s0);  
MUX MUX_03(y,y01,y02,s1);  
  
endmodule
```



# Specifying connectivity

- There are two alternate ways of specifying connectivity:

- \* Positional association

- The connections are listed in the same order

```
add A1 (c_out, sum, a, b, c_in);
```

- \* Explicit association

- May be listed in any order

```
add A1 (.in1(a), .in2(b), .cin(c_in), .sum(sum), .cout(c_out));
```

# Port connectivity

```
module subMod(out1,out2,in1,in2);  
  ...  
endmodule
```

```
module Mod;
```


```
  //positional association  
  subMod M1(O1,O2,I1,I2);
```

```
  //explicit association  
  subMod M2(.out1(O1),.out2(O2),.in1(I1),.in2(I2));
```

```
endmodule
```
 
# Testbench

- A procedural block which executes only once
- Used for simulation
- Generates clock, reset, and the required test vectors



# How to write testbench

- Create a dummy module
  - \* Declare inputs to the module-under-test (MUT) as 'reg' and the outputs as 'wire'
  - \* Instantiate the MUT
- Initialization
  - \* Assign some known values to the MUT inputs
- Generate the clock
- Use simulator directives to print the results

# Testbench

```
module top;
  reg a,b,c,d;
  reg s1, s2;
  wire y;
  mux4x1 mux_inst(y,a,b,c,d,s1,s2);

  initial begin
    a=b=c=d=s1=s2=1'b0;
    $monitor("y=%b a=%b b=%b c=%b d=%b s0=%b s1=%b"
             time=%2d,y,a,b,c,d,s0,s1,$time);
    #1 a=1'b1; #1 s1=1'b1; #1 a=1'b0;
    #1 c=1'b1; #1 s0=1'b1;
    #10 $finish;
  end
endmodule
```

# Logic values

- 0,1 – Binary value
- X – Unknown value
- Z – High impedance state
- All unconnected nets are set to 'z'
- All registers variables are set to 'x'

# Functional table for primitive gates

AND				
	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

XOR				
	0	1	x	z
0	0	1	x	x
1	1	0	x	x
x	x	x	x	x
z	x	x	x	x



# Verilog operator

- Arithmetic operator: `*`, `/`, `+`, `-`
- Logical operator: `!`, `&&`, `||`
- Relational operator: `>`, `<`, `>=`, `<=`, `==`, `!=`
- Bitwise operator: `&`, `|`, etc.
- Reduction operator: Operate on all the bits within a word (`&`, `~&`, etc.)
- Shift operator: `<<`, `>>`
- Concatenation operator: `{}`
- Replication operator: `{}`
- Conditional: `expr? exp1 : exp2;`

# Data types

- Net: Represents the continuous updating of outputs with respect to their changing inputs.
  - \* `wire, supply0, supply1`
  - \* `wire wire01,wire02;`
- reg: Has to be assigned values explicitly. Value is held until a new assignment is made
  - \* `reg out1, out2;`
- Integer: `integer intparam;`
- Real: `real realparam;`
- Vector: `reg [3:0] output;`
- Arrays: `reg data [7:0];`
- 1K memory of 16 bit elements –  
`reg [15:0] mem16_1024 [0:1023]`

## Data type: wire

- wire elements are used to connect input and output ports of a module instantiation together with some other element in your design.
- wire elements are used as inputs and outputs within an actual module declaration.
- wire elements must be driven by something, and cannot store a value without being driven.
- wire elements cannot be used as the left-hand side of an = or <= sign in an always@ block.
- wire elements are the only legal type on the left-hand side of an assign statement.
- wire elements are a stateless way of connecting two pieces in a Verilog-based design.
- wire elements can only be used to model combinational logic.
- wire, wor, wand, tri, supply0, supply1


## Data type: reg

- It can be connected to the input port of a module instantiation.
- It cannot be connected to the output port of a module instantiation.
- It can be used as outputs within an actual module declaration.
- It cannot be used as inputs within an actual module declaration.
- It is the only legal type on the left-hand side of an always@ block = or <= sign.
- It is the only legal type on the left-hand side of an initial block = sign (used in Test Benches).
- It cannot be used on the left-hand side of an assign statement.
- It can be used to create registers when used in conjunction with always@(posedge Clock) blocks.
- It can, therefore, be used to create both combinational and sequential logic.

# Data type: reg

- Different 'register' types supported for synthesis:
  - \* reg, integer
- The 'reg' declaration explicitly specifies the size.
  - \* reg x, y; // single-bit register variables
  - \* reg [15:0] bus; // 16-bit bus, bus[15] MSB
- For 'integer', it takes the default size, usually 32-bits.
  - \* Synthesizer tries to determine the size.
- Arithmetic expressions
  - \* An 'integer' is treated as a 2's complement signed integer.
  - \* A 'reg' is treated as an unsigned quantity.
- General rule of thumb
  - \* reg used to model actual hardware registers such as counters, accumulator, etc.
  - \* integer used for situations like loop counting.

# Port connectivity

 

# Specifying const values

- Values can be specified in sized or unsized form
  - \* Syntax for sized form: `<size>'<base><number>`
- Examples
  - \* `4'b0011` //4-bit binary number
  - \* `12'hA2D` //hexadecimal number
  - \* `12'hCx5` //1100 xxxx 0101 in binary
  - \* `25` //signed number 32 bits
  - \* `1'b0` //Logic 0
  - \* `1'b1` //Logic 1

# Parameters

- A parameter is a constant with name
- No size is allowed to be specified for a parameter
- The size gets decided from the constant itself. 32 bits if nothing is specified.
- Examples
  - \* `parameter HI = 25, LO = 5;`
  - \* `parameter up = 1'b0;`



# Note

- For all primitive gates:
  - \* The output port must be connected to a net.
  - \* The input port must be connected to a net or reg.
  - \* Can have only single output but any number of inputs
- Boolean true/false
  - \* true is equivalent to 1'b1;
  - \* false is equivalent to 1'b0;

# Simple AND gate


```
module simple_and(out, A, B);  
    input A, B;  
    output out;  
    assign out = A & B;  
endmodule
```

# Two level circuits

```
module two_level (a, b, c, d, f);  
input a, b, c, d;  
output f;  
wire t1, t2;  
    assign t1 = a & b;  
    assign t2 = ~(c | d);  
    assign f = t1 ^ t2;  
endmodule
```


## Example: wire

```
module using_wire (A, B, C, D, f);  
  input A, B, C, D;  
  output f;  
  // net f declared as 'wire'  
  wire f;  
  assign f = A & B;  
  assign f = C | D;  
endmodule
```

 


## Example: wire

```
module using_wire (A, B, C, D, f);  
  input A, B, C, D;  
  output f;  
  // net f declared as 'wand'  
  wand f;  
  assign f = A & B;  
  assign f = C | D;  
endmodule
```

 

 
# MUX : Behavioral form

```
module MUX(out, A, B, SEL);  
    output out;  
    reg out;  
    input A, B, SEL;  
  
    always @(SEL, A, B)  
        if(S)  
            out=A;  
        else  
            out=B;  
  
endmodule
```


 
# MUX : Continuous assignment

```
module MUX(out, A, B, SEL);  
    output out;  
    input A, B, SEL;  
  
    assign out = SEL ? A : B;  
  
endmodule
```



## 8-bit adder

```
module adder(sum,cout,in1,in2,cin);  
    input [7:0] in1, in2;  
    input cin;  
    output [7:0] sum;  
    output cout;  
    assign #20 {cout,sum} = in1 + in2 + cin;  
endmodule
```



# Description styles

- Data flow
  - \* Continuous assignment
- Behavioral
  - \* Procedural assignment
    - Blocking
    - Non-blocking

# Description styles: Continuous assignment

- Identified by the word 'assign'
- `assign a = b & c;`
- The 'net' is being assigned on the LHS, i.e. LHS must be of 'net' type
- Expression is on the RHS. RHS may contain both 'reg' or 'net'.
- Assignment is continuously active
- Exclusively used to model combinational logic
- A module can contain any number of continuous assignment statements

# Behavioral style: Procedural assignment

- A region of code containing sequential statements
- The statements execute in the order they are written
- Two types of procedural blocks
  - \* 'always' – Continuous loop that never terminate
  - \* 'initial' – Executed once at the beginning of simulation

# initial block

- An initial block consists of a statement or a group of statements enclosed in **begin** ... **end** which will be executed only once at simulation time 0.
- Multiple initial blocks in an design are executed in parallel
- Normally used for initialization, monitoring, generating wave forms (eg, clock pulses) and processes which are executed once in a simulation.

# Procedural assignment: always

- A module can contain any number of 'always' block
- Syntax for 'always' block

```
always @(event_expression)
begin
    statement
end
```

- @(event\_expression) is required for both combinational and sequential logic

# only 'reg' can be assigned within 'always'

- 'always' block executes only when the event expression triggers
- At other time block is doing nothing
- An object being assigned to must therefore remember the last value assigned
- any kind of variable may appear in the event expression

# Sequential statements

- `begin`  
    `sequential_statements`  
`end`
- `if(expression)`  
    `sequential_statement`  
    `[else`  
        `sequential_statement]`
- `case(expression)`  
    `expr: sequential_statement`  
    `default: sequential_statement`  
`endcase`

## Sequential statements (contd)

- `forever`  
    `sequential_statement`
- `repeat(expression)`  
    `sequential_statement`
- `while(expression)`  
    `sequential_statement`
- `for(expr1;expr2;expr3)`  
    `sequential_statement`



# Blocking vs Non-blocking

- Sequential statements within procedural blocks can use two types of assignments
  - \* Blocking assignment : Use the '=' operator
  - \* Nonblocking assignment : Use the '<=' operator

# Blocking


- Most commonly used type
- The target of assignment gets updated before the next sequential statement in the procedural block
- It blocks the execution of the statements following it
- Recommended style for modeling combinational logic

# Nonblocking

- The assignment to the target gets scheduled for the end of the simulation cycle
  - \* Normally occurs at the end of the sequential block
  - \* Statement subsequent to the instruction under consideration are not blocked by the assignment
- Recommended style for modeling sequential logic
  - \* Can be used to assign several 'reg' type variable synchronously, under the control of a common clock.
- A variable cannot appear as the target of both blocking and a nonblocking assignment
 
# Example

```
reg aout, bout, cout;  
wire ain, bin, cin;  
always @(negedge clk)  
  
begin  
    aout<=ain;  
    bout<=aout+1;  
    cout<=bout+1;  
end
```



# Example


```
reg aout, bout, cout;  
wire ain, bin, cin;
```

```
always @(negedge clk)  
begin
```

```
    aout<=ain;  
    bout<=bin;  
    cout<=cin;
```

```
end
```
 
```
assign bin=aout+1;  
assign cin=bout+1;
```



# Example

```
reg aout, bout, cout;  
wire ain, bin, cin;
```


```
always @(negedge clk)  
    aout<=ain;
```

```
assign bin=aout+1;
```

```
always @(negedge clk)  
    bout<=bin;
```


```
assign cin=bout+1;
```
 
```
always @(negedge clk)  
    cout<=cin;
```


 
# Example

```
reg aout, bout, cout;  
wire ain, bin, cin;  
  
always @(negedge clk)  
begin  
    aout=ain;  
    bout=bin;  
    cout=cin;  
end  
  
assign bin=aout+1;  
assign cin=bout+1;
```




# Example

```
reg aout, bout, cout;  
wire ain, bin, cin;
```

```
always @(negedge clk)  
begin  
    aout=ain;  
    bout=bin;  
    cout=cin;  
end
```
 
```
assign bin=aout+1;  
assign cin=bout+1;
```



NOT CORRECT



# Counter design

```
module counter(out,en,reset,clk);
    output [3:0] out;
    reg      [3:0] out;
    input    en,reset,clk;
    wire     en,reset,clk;

    always @(posedge clk)
    begin :COUNTER
        if(reset == 1'b1) out = 4'b0000;
        else if(en == 1'b1) out = out + 1;
    end // end of COUNTER

endmodule
```

# Clock generator

```
module cklGen(out);  
    output out;  
    reg     out;  
  
    initial begin  
        out = 1'b0;  
    end  
  
    always  
    begin :CLK  
        out = #1 ~out;  
    end // end of CLK  
  
endmodule
```

# Testbench

```
module top;
  wire clk;
  clkGen M1(clk);
  counter M2(out,reset,en,clk);

  initial begin
    $monitor("out=%d time=%d\n",out,$time);
    reset=1'b0; en=1'b0;
    #5 en=1'b1;
    #100 $finish;
  end
endmodule
```

# Simulator directives

- `$display` – Similar to `printf`
- `$monitor` – Similar to `$display`, but prints whenever the value of some variables in the given list changes
- `$finish` – Stop simulation
- `$dumpfile`, `$dumpvar`, `$readmemb`, `$readmemh`

# Synchronous up-down counter

```
module counter (mode, clr, ld, d_in, clk, count);  
  input mode, clr, ld, clk; input [0:7] d_in;  
  output [0:7] count;  
  reg [0:7] count;  
  always @ (posedge clk)  
    if(ld)  
      count <= d_in;  
    else if(clr)  
      count <= 0;  
    else if(mode)  
      count <= count + 1;  
    else  
      count <= count - 1;  
endmodule
```

# Multiple clocks

```
module multiple_clk (clk1, clk2, a, b, c, f1, f2);  
  input clk1, clk2, a, b, c;  
  output f1, f2;  
  reg f1, f2;  
  
  always @ (posedge clk1)  
    f1 <= a & b;  
  
  always @ (negedge clk2)  
    f2 <= b ^ c;  
  
endmodule
```

# Multiple edges of the clk

```
module multi_phase_clk (a, b, f, clk);  
  input a, b, clk;  
  output f;  
  reg f, t;  
  
  always @ (posedge clk)  
    f <= t & b;  
  
  always @ (negedge clk)  
    t <= a | b;  
  
endmodule
```

# Ring counter

```
module ring_counter (clk, init, count);
  input clk, init;
  output [7:0] count;
  reg [7:0] count;
  always @ (posedge clk)
  begin
    if(init)
      count = 8'b10000000;
    else begin
      count = count << 1;
      count[0] = count[7];
    end
  end
end
endmodule
```





## Ring counter (contd.)

```
module ring_counter (clk, init, count);
  input clk, init;
  output [7:0] count;
  reg [7:0] count;
  always @ (posedge clk)
  begin
    if(init)
      count = 8'b10000000;
    else begin
      count <= count << 1;
      count[0] <= count[7];
    end
  end
end
endmodule
```

## Ring counter (contd.)

```
module ring_counter (clk, init, count);
    input clk, init;
    output [7:0] count;
    reg [7:0] count;
    always @ (posedge clk)
    begin
        if(init)
            count = 8'b10000000;
        else begin
            count = {count [6:0], count [7]};
        end
    end
endmodule
```

# Finite State Machine

  

# FSM: Traffic Light Controller

- Simplifying assumptions made
- Three lights only (RED, GREEN, YELLOW)
- The lights glow cyclically at a fixed rate
  - \* Say, 10 seconds each
  - \* The circuit will be driven by a clock of appropriate frequency

# Traffic light controller

```
module traffic_light (clk, light);  
input clk;  
output [0:2] light;  
reg [0:2] light;  
parameter S0=0, S1=1, S2=2;  
parameter RED=3'b100, GREEN=3'b010,  
YELLOW=3'b001;  
reg [0:1] state;
```

# Traffic light controller

```
module traffic_light (clk, light);
input clk;
output [0:2] light;
reg [0:2] light;
parameter S0=0, S1=1, S2=2;
parameter RED=3'b100, GREEN=3'b010,
YELLOW=3'b001;
reg [0:1] state;
always @ (posedge clk)
case(state)
S0: begin //RED
light <= YELLOW;
state <= S1;
end
```

# Traffic light controller

```
module traffic_light (clk, light);  
  input clk;  
  output [0:2] light;  
  reg [0:2] light;  
  parameter S0=0, S1=1, S2=2;  
  parameter RED=3'b100, GREEN=3'b010,  
  YELLOW=3'b001;  
  reg [0:1] state;  
  always @ (posedge clk)  
  case(state)  
    S0: begin //RED  
      light <= YELLOW;  
      state <= S1;  
    end  
    S1: begin //YELLOW  
      light <= GREEN;  
      state <= S2;  
    end  
  endcase  
end
```

# Traffic light controller

```
module traffic_light (clk, light);
input clk;
output [0:2] light;
reg [0:2] light;
parameter S0=0, S1=1, S2=2;
parameter RED=3'b100, GREEN=3'b010,
YELLOW=3'b001;
reg [0:1] state;
always @ (posedge clk)
case(state)
S0: begin //RED
    light <= YELLOW;
    state <= S1;
end
S1: begin //YELLOW
    light <= GREEN;
    state <= S2;
end
S2: begin //GREEN
    light <= RED;
    state <= S0;
end
end
```



# Traffic light controller

```
module traffic_light (clk, light);
input clk;
output [0:2] light;
reg [0:2] light;
parameter S0=0, S1=1, S2=2;
parameter RED=3'b100, GREEN=3'b010,
YELLOW=3'b001;
reg [0:1] state;
always @ (posedge clk)
case(state)
  S0: begin //RED
    light <= YELLOW;
    state <= S1;
  end
  S1: begin //YELLOW
    light <= GREEN;
    state <= S2;
  end
  S2: begin //GREEN
    light <= RED;
    state <= S0;
  end
default: begin
  light <= RED;
  state <= S0;
end
endcase
endmodule
```

## Traffic light controller (contd.)

```
module traffic_light_nonlatched_op
  (clk, light);
  input clk; output [0:2] light;
  reg [0:2] light;
  parameter S0=0, S1=1, S2=2;
  parameter RED=3'b100,
  GREEN=3'b010, YELLOW=3'b001;
  reg [0:1] state;
```

## Traffic light controller (contd.)

```
module traffic_light_nonlatched_op
  (clk, light);
input clk; output [0:2] light;
reg [0:2] light;
parameter S0=0, S1=1, S2=2;
parameter RED=3'b100,
GREEN=3'b010, YELLOW=3'b001;
reg [0:1] state;
always @ (posedge clk)
case(state)
  S0: state <= S1;
  S1: state <= S2;
  S2: state <= S0;
  default: state <= S0;
endcase
```

## Traffic light controller (contd.)

```
module traffic_light_nonlatched_op
  (clk, light);
  input clk; output [0:2] light;
  reg [0:2] light;
  parameter S0=0, S1=1, S2=2;
  parameter RED=3'b100,
  GREEN=3'b010, YELLOW=3'b001;
  reg [0:1] state;
  always @ (posedge clk)
  case(state)
    S0: state <= S1;
    S1: state <= S2;
    S2: state <= S0;
    default: state <= S0;
  endcase
```

```
always @ (state)
  case(state)
    S0: light = RED;
    S1: light = YELLOW;
    S2: light = GREEN;
    default: light = RED;
  endcase
endmodule
```

# Verilog: function & task

- These allow the designers to abstract Verilog code that is used at many places in the design
- function
  - \* Can enable other functions but no task
  - \* Executes in 0 simulation time
  - \* Must have at least one input argument
  - \* Returns a single value
- task
  - \* Can enable other functions and tasks
  - \* May execute in non-zero simulation time
  - \* May have zero or more argument
  - \* Does not return value but can pass value through inout or output

## Example: Task

```
module op;
...
always @(...) begin
    ...
    bitwiseOpr(AB_AND,A,B)
end

task bitwiseOpr
input A,B;
output AB_AND
begin
    AB_AND = A & B;
end
endtask
endmodule
```

## Example: Function


```
module op;  
  reg X;  
  always @(...) begin  
    ...  
    X=bitwiseOpr(A,B)  
  end  
  
  function bitwiseOpr;  
    input A,B;  
    begin  
      bitwiseOpr = A & B;  
    end  
  endfunction  
  ...  
endmodule
```

# Verilog PLI

- The Verilog PLI is a simulation interface
  - \* Reads/modifies simulation data structures
  - \* Does not read Verilog source code
  - \* Does not work with synthesis compilers or other tools
- The PLI is a protecting layer between user programs and simulation data structure
  - \* Indirect access through PLI libraries
    - C program cannot directly read or modify the simulation data
    - Protects the simulator from bad C programs
    - Protects C programs from bad Verilog code



# Verilog PLI

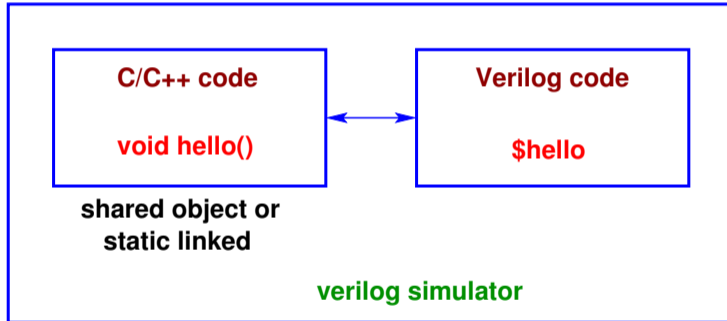


## Example: GCD in C

```
int GCD(int A, int B){
    int done=0; int tmpA = A, tmpB = B;
    while(done != 1){
        if(A < B){
            int tmp = B; B = A; A = tmp;
        }else if(B != 0){
            A = A - B;
        }else{
            done = 1;
        }
    }
    return A;
}
```


## Example: GCD in verilog

```
module GCD#(parameter W=8) (out, A, B);
  input [w-1:0] A, B; output [w-1:0] out;
  reg [w-1:0] tmpA, tmpB, out, swap; integer done;
  always @(*) begin
    done=0; tmpA = A; tmpB = B;
    while(!done) begin
      if(tmpA<tmpB)
        swap = tmpA; tmpA = tmpB; tmpB = swap;
      else if(tmpB!=0)
        tmpA = tmpA - tmpB;
      else
        done = 1;
    end
    out = tmpA
  end
endmodule
```


# GCD: Top level view

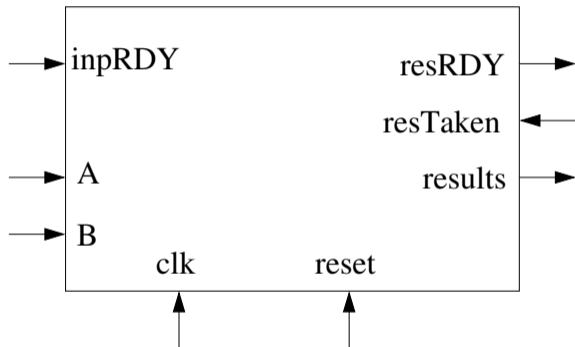

# GCD: Datapath & Control module

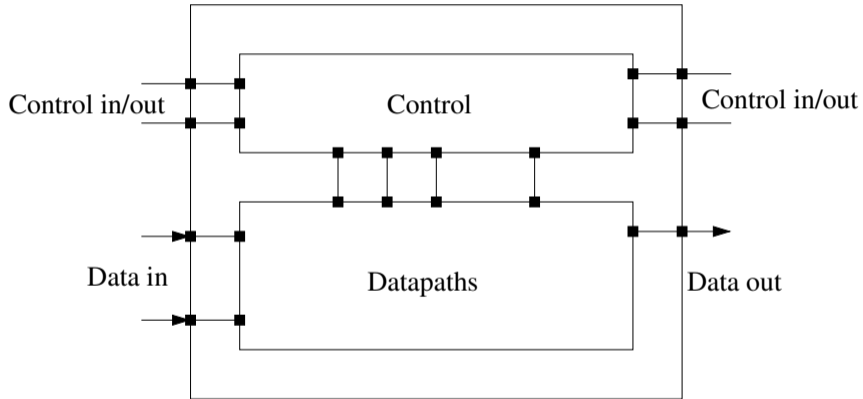

# GCD: Datapath & Control module

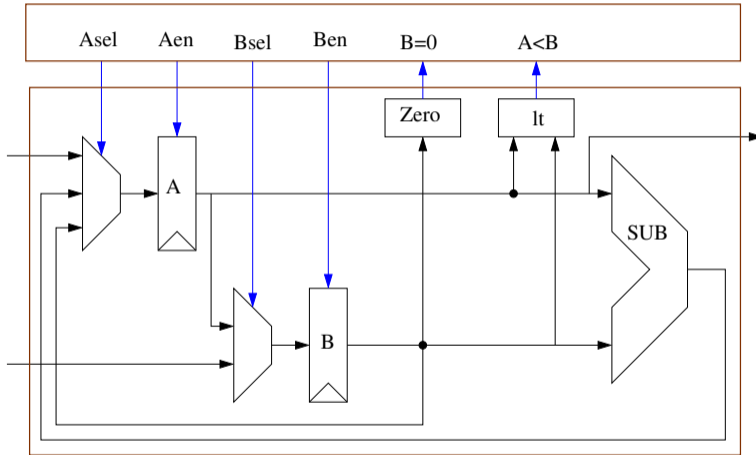


# GCD: Datapath module

```
module GCDDP#(parameter W=8) (.....){
    input [w-1:0] A, B; output [w-1:0] results;
    input Aen, Ben, Asel, Bsel;
    output bZero, A_lt_B;
    input clk;

    AMUX();
    AFF();
    BMUX();
    BFF();
    B_EQ_0();
    LessThan();
    Subtractor();

endmodule
```

# GCD: FSM

 



# GCD: Control module

```
module GCDControl (.....)
  input inpRDY, resTaken; output resRDY;
  output Aen, Ben, Asel, Bsel;
  input bZero, A_lt_B;
  input clk, reset;

  reg nextState; wire state
  DFF(nextState -> state);
  always @(*)
    WAIT: set various signal lines
    CALC: set various signal lines
    DONE: set various signal lines
endcase
```

# GCD: Control module

```
always @(*)
case(state)
  WAIT: if(inpRDY) nextState = CALC
  CALC: if(bZero) nextState = DONE
  DONE: .....
  default: nextState = state
endcase
endmodule
```


# FIR Filter

- Let us consider car engine temperature ( $X$ ) in every second: 180, 181, 180, 240, 180, 181
- 240 is spurious value, needs to be ignored
- $Y(t) = c_0 \times x(t) + c_1 \times x(t - 1) + c_2 \times x(t - 2)$


# FIR Filter




# FIR Filter

 


# FIR Filter

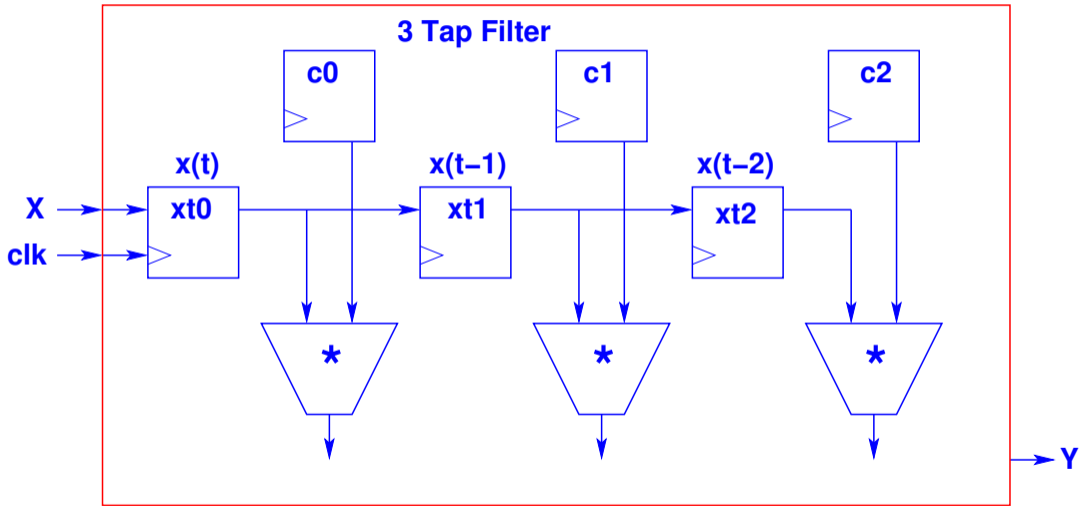

# FIR Filter

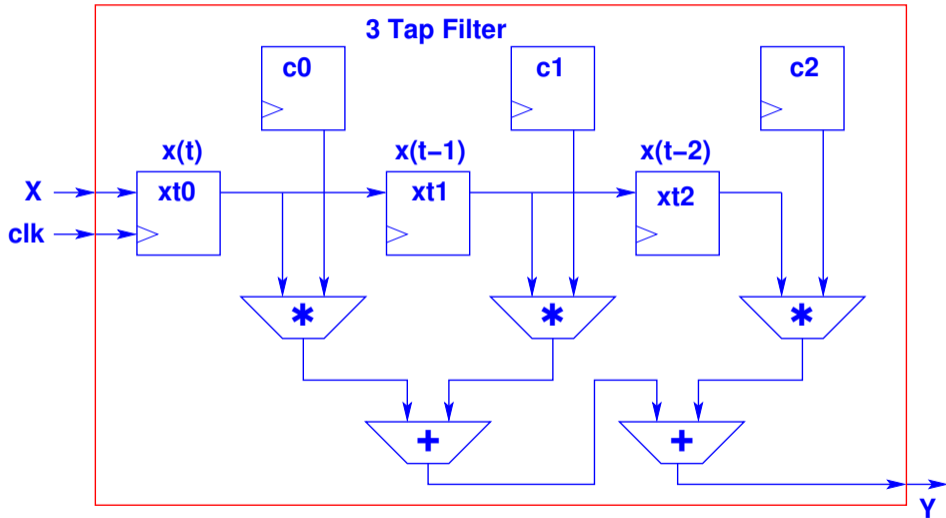

# FIR Filter

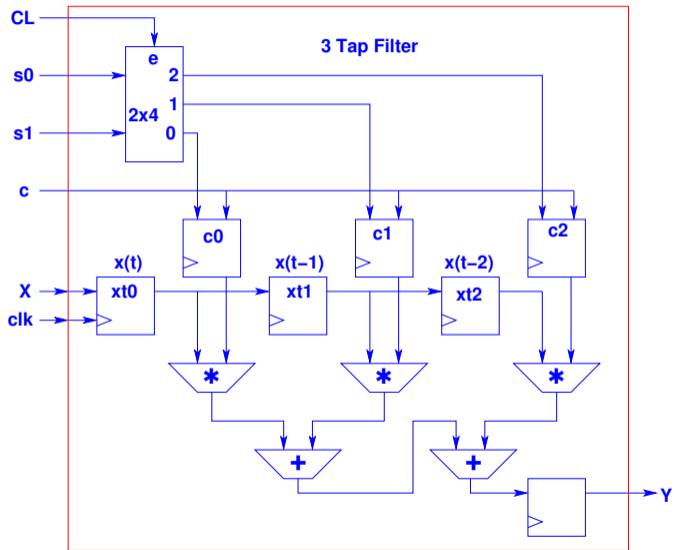



**Thank you!**