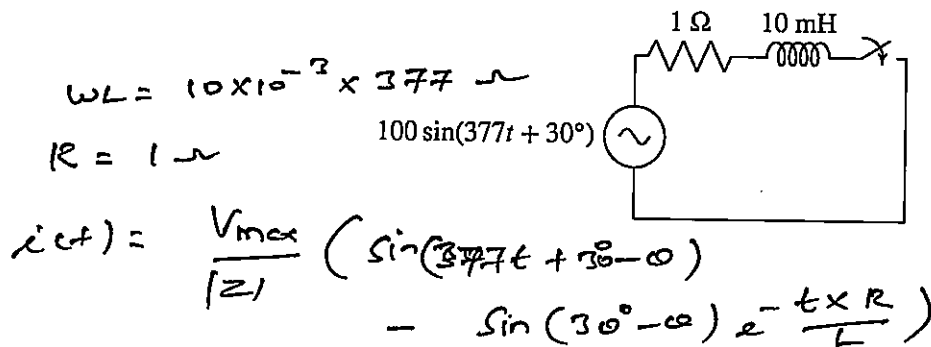


There are 5 problems. They carry equal marks.

$$(5 \times 2 = 10)$$


1. In the circuit shown below, the switch is closed at $t = 0$. Find the value of DC offset of the current at the time of switching.



$$i_{dc} = -\frac{100}{|Z|} \sin(30^\circ - \phi) \quad \text{at } t=0$$

$$i_{dc} = 18.1748 \text{ A}$$

2. A three phase balanced source is applied to the load shown below. The phase sequence is RYB. Find $\left| \frac{I_R}{I_Y} \right|$.

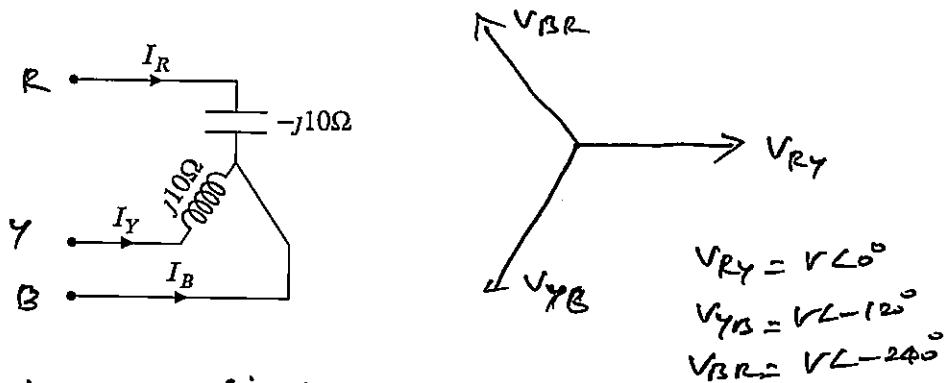

$$-V_{RY} + I_R(-j10) - I_Y(j10) = 0 \quad \text{--- (1)}$$

$$-V_{YB} + I_Y \times j10 = 0 \quad \text{--- (2)}$$


$$\textcircled{2} \Rightarrow I_Y = \frac{V \angle -120^\circ}{j10} = \frac{V}{10} \angle -210^\circ$$

From (1)

$$I_R = \frac{V}{10} \angle -150^\circ$$

$$\left| \frac{I_R}{I_Y} \right| = \frac{\frac{V}{10}}{\frac{V}{10}} = 1$$

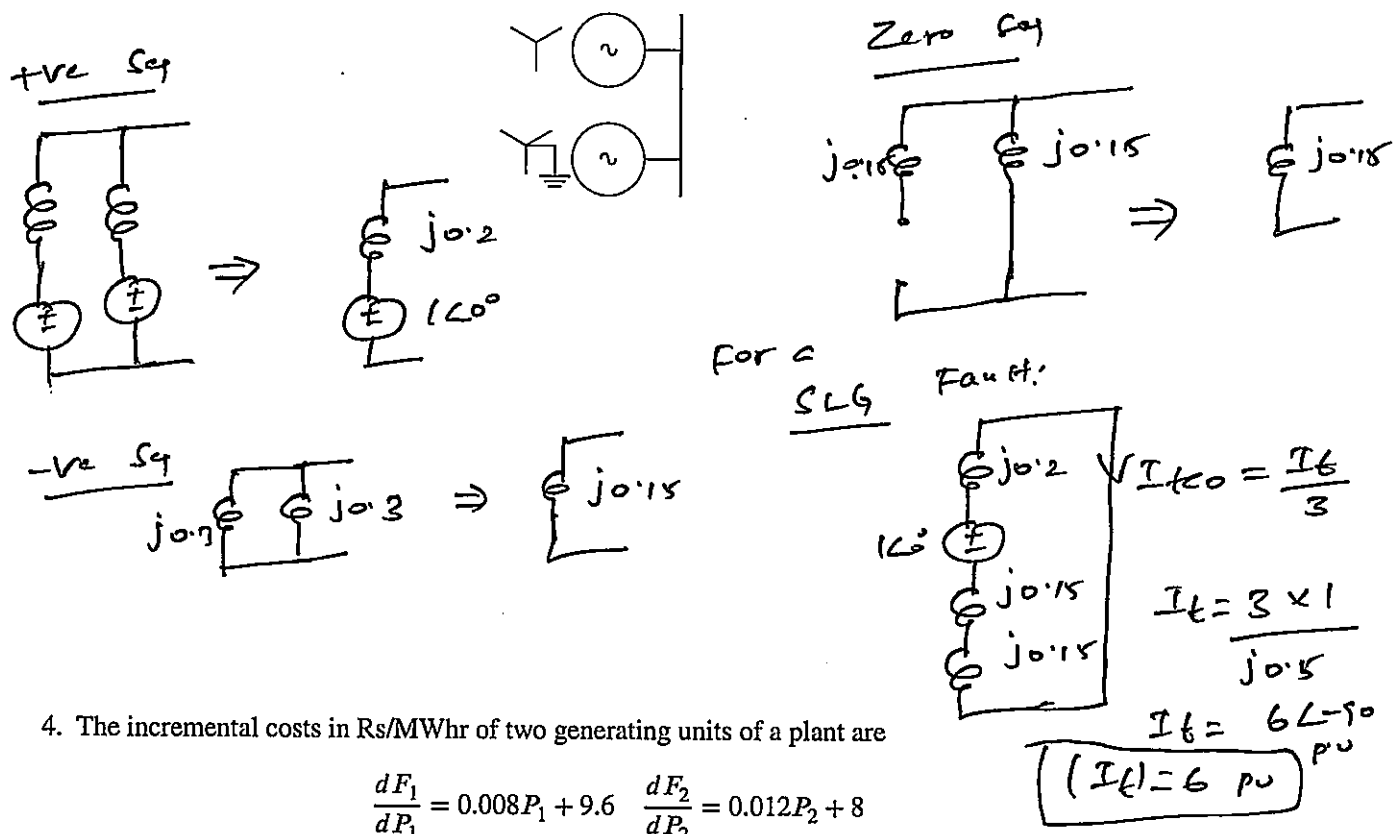3. Two identical unloaded generators are connected in parallel as shown in the figure. Both the generators are having positive, negative and zero sequence impedances of $j0.4$ p.u., $j0.3$ p.u. and $j0.15$ p.u., respectively. If the pre-fault voltage is 1 p.u., find the fault current in per unit for a line-to-ground (L-G) fault at the terminals of the generators.



4. The incremental costs in Rs/MWhr of two generating units of a plant are

$$\frac{dF_1}{dP_1} = 0.008P_1 + 9.6 \quad \frac{dF_2}{dP_2} = 0.012P_2 + 8$$

Calculate the saving in Rs/hr if a load of 200 MW is shared optimally rather than equally.

For optimal scheduling

$$\frac{dF_1}{dP_1} = \frac{dF_2}{dP_2}$$

$$P_1 + P_2 = 200$$

By solving this

$$P_1 = 40 \text{ MW}$$

$$P_2 = 160 \text{ MW}$$

For equal sharing


$$P_1 = 100 \text{ MW}$$

$$P_2 = 100 \text{ MW}$$

$$\text{Saving} = \int_{40}^{100} \left(\frac{dF_1}{dP_1} \right) dP_1 + \int_{160}^{100} \left(\frac{dF_2}{dP_2} \right) dP_2$$

$$\text{Saving} = 36 \text{ Rs/hr}$$

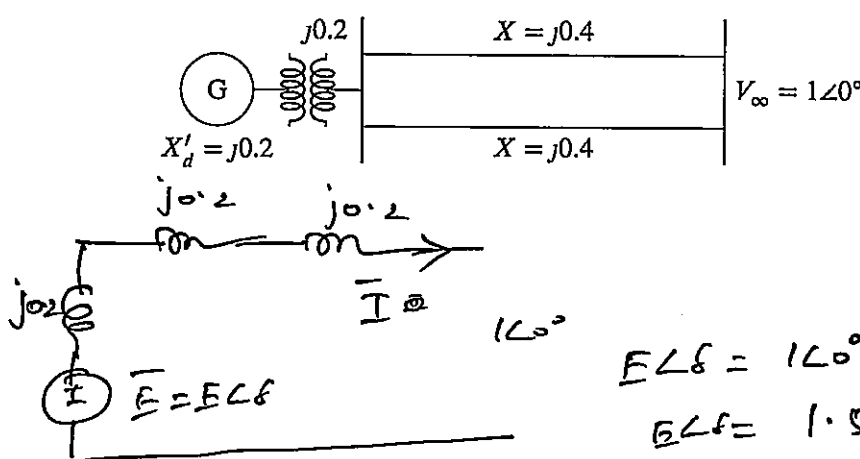5. In the single machine infinite bus system shown below, the generator is delivering the real power of 1 p.u. at 0.8 power factor lagging to the infinite bus. Find the power angle of the generator in degrees.



$$|\bar{I}| = \frac{1}{1 \times 0.8}$$

$$= \left(\frac{P}{V \times \cos \phi} \right)$$

$$\bar{I} = \frac{1}{0.8} \angle -\cos^{-1} 0.8$$

$$E \angle \delta = 1 \angle 0^\circ + \bar{I} \times j0.6$$

$$E \angle \delta = 1.57 \angle 22.48^\circ$$

$$\boxed{\delta = 22.48^\circ}$$