

Indian Institute of Technology Patna
Department of Electrical Engineering
EE381 - Power Systems

Autumn - 2023


Mid Semester Exam - Solution.

September 30, 2023

There are 5 questions. They carry equal marks.

(5 × 6 = 30)

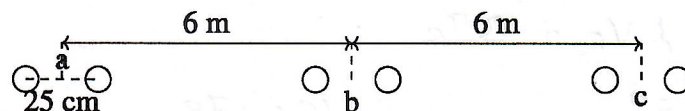1. Determine the total inductance and capacitance of the single circuit, two-bundle and 200 km long line as shown below. The diameter of each conductor is 5 cm. ($\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$)



$$GMD = \sqrt[3]{D_{ab} D_{bc} D_{ca}} = \sqrt[3]{6 \times 6 \times 12} = 7.56 \text{ m}$$

$$GMR_L = \sqrt[2]{r' \times d} = \sqrt[2]{0.7788 \times \frac{5}{2} \times 10^{-2} \times 25 \times 10^{-2}}$$

$$GMR_L = 0.07 \text{ m}$$

$$GMR_c = \sqrt[2]{r \times d} = \sqrt[2]{\frac{5}{2} \times 10^{-2} \times 25 \times 10^{-2}} = 0.08 \text{ m}$$

$$L = 2 \times 10^{-7} \ln \left(\frac{GMD}{GMR_L} \right) = 9.4 \times 10^{-7} \text{ H/m}$$

$$L = 0.94 \text{ mH/km}$$

$$C = \frac{2\pi\epsilon_0}{\ln \left(\frac{GMD}{GMR_c} \right)} = 1.22 \times 10^{-11} \text{ F/m}$$

$$C = 0.0122 \text{ }\mu\text{F/km}$$

Total Inductance

$$L = L \times \text{length} = 0.94 \times 200 \text{ mH}$$

$$\approx 188 \text{ mH} = 0.188 \text{ H}$$

$$L \approx 0.19 \text{ H}$$

$$C = C \times 200 = 2.44 \text{ }\mu\text{F}$$

2. A 250 km long, three phase, 50 Hz transmission line has the following constants.

$$A = D = 0.9 \angle 1^\circ$$

$$B = 120 \angle 72^\circ \Omega$$

$$C = 0.001 \angle 90^\circ \text{ S}$$

The sending end voltage is 230 kV. Find

- the receiving end voltage and the line charging current when there is no load.
- the sending end voltage angle at which the maximum real power can be transferred.
(Hint: Real power flow is a function of voltage angle. Take V_R as reference.)

$$a) \quad V_S / \text{phase} = \frac{230}{\sqrt{3}} = 132.79 \text{ kV}$$

$$V_S = AV_R + BI_R$$

$$\text{Since } I_R = 0, \quad V_R = \frac{V_S}{A} = \frac{132.79}{0.9 \angle 1^\circ} = 147.54 \angle 1^\circ \text{ kV/phase}$$

$$V_R = 255.56 \text{ kV (Line)}$$

$$I_S = CV_R = 147.55 \angle 89^\circ \text{ A}$$

$$b) \quad \text{Let } V_S = |V_S| \angle \delta, \quad V_R = |V_R| \angle 0^\circ, \quad A = |A| \angle \alpha, \\ B = |B| \angle \beta$$

$$V_S = AV_R + BI_R$$

$$\text{From this eq, } I_R = \frac{V_S - AV_R}{B}$$


$$S_R = \{V_R I_R^*\} \quad P_R = \text{Re} \{S_R\} = \text{Re} \{V_R I_R^*\}$$

$$P_R = \text{Re} \left\{ V_R \angle 0^\circ \left(\frac{V_S \angle \delta - |A| \angle \alpha V_R \angle 0^\circ}{|B| \angle \beta} \right)^* \right\}$$

$$P_R = \frac{V_R V_S}{|B|} \cos(\beta - \delta) - \frac{V_R^2 |A|}{|B|} \cos(\beta - \alpha)$$

$$\frac{dP_R}{d\delta} = 0 \quad ; \quad \boxed{\beta = \delta} \quad \text{Hence } \boxed{\delta = 72^\circ}$$

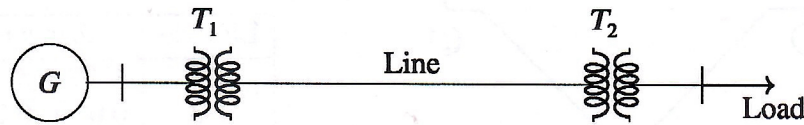3. The schematic diagram of a radial transmission system is shown below.



T_1 : 100 MVA, 11/220 kV. $X = 12\%$

T_2 : 100 MVA, 220/66 kV. $X = 10\%$

Line: $j100 \Omega$.

Load: 60 MW at 0.9 pf lagging.

If the load voltage is to be maintained at 60 kV, what will be the terminal voltage in kV of the generator?

Let us choose Base MVA = 100 MVA
Base kV = 220 kV (on Transmission line)

$$\text{Base kV on Load} = \frac{220 \times 66}{220} = 66 \text{ kV}$$

$$\text{Base kV on G} = \frac{220 \times 11}{220} = 11 \text{ kV}$$

$$X_{T1} = j0.12 \times \left(\frac{100}{100}\right) \times \left(\frac{220}{220}\right)^2 = j0.12$$

$$X_{T2} = j0.1 \times \left(\frac{100}{100}\right) \times \left(\frac{66}{66}\right)^2 = j0.10$$

$$\text{OR } j0.1 \times \left(\frac{100}{100}\right) \times \left(\frac{220}{220}\right)^2 = j0.10$$


$$X_{\text{Line}} = j100 \times \frac{100}{220^2}$$

$$X_{\text{Line}} = j0.2066 \text{ p.u.}$$

$$P_L = \frac{60}{100} = 0.6 \text{ p.u.}, \quad V_L = \frac{60}{66} = 0.91 \text{ p.u.}$$

$$I_L = \frac{0.6}{0.91 \times 0.9} = 0.7326 \text{ p.u.}$$
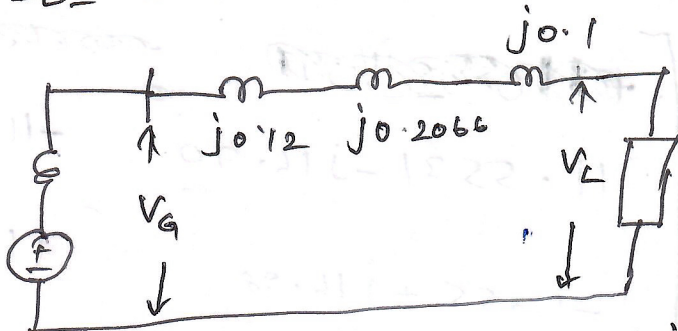
$$\bar{I}_L = 0.7326 \angle -\cos^{-1}(0.9) \text{ p.u.}$$




$$\bar{V}_G = \bar{V}_L + \bar{I}_L \times (j0.12 + j0.2066 + j0.1)$$

$$\bar{V}_G = 1.0834 \angle 15.04^\circ \text{ p.u.}$$

$$V_G = 1.0834 \times 11 = 11.92 \text{ kV}$$

4. Consider the three node network.

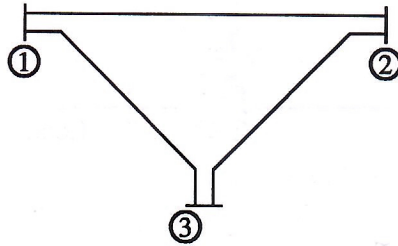

Line No	Z in p.u	$\frac{Y}{2}$ in p.u
1-2	$0.02 + j0.06$	$j0.03$
1-3	$0.08 + j0.024$	$j0.025$
2-3	$0.06 + j0.018$	$j0.02$

(a) Form the Y_{bus} matrix.

(b) Modify the the Y_{bus} matrix by eliminating node ③.

$$a) Y_{11} = \frac{1}{0.02 + j0.06} + \frac{1}{0.08 + j0.024} + j0.03 + j0.025 = 16.47 - j18.39$$

$$Y_{12} = -\frac{1}{0.02 + j0.06} = -5 + j15 \quad ; \quad Y_{13} = -11.47 + j3.44$$

$$Y_{21} = Y_{12} \quad ; \quad Y_{22} = 20.29 - j19.54 \quad ; \quad Y_{23} = -15.29 + j4.6$$


$$Y_{31} = Y_{13} \quad ; \quad Y_{32} = Y_{23} \quad ; \quad Y_{33} = 26.76 - j7.98$$

$$Y_{bus} = \begin{bmatrix} 16.47 - j18.39 & -5 + j15 & -11.47 + j3.44 \\ -5 + j15 & 20.29 - j19.54 & -15.29 + j4.6 \\ -11.47 + j3.44 & -15.29 + j4.6 & 26.76 - j7.98 \end{bmatrix}$$

b) After elimination ③

$$Y_{bus}^{(Mod)} = \begin{bmatrix} 11.5531 - j16.90 & -11.55 + j16.98 \\ -11.55 + j16.98 & 11.5531 - j16.90 \end{bmatrix}$$

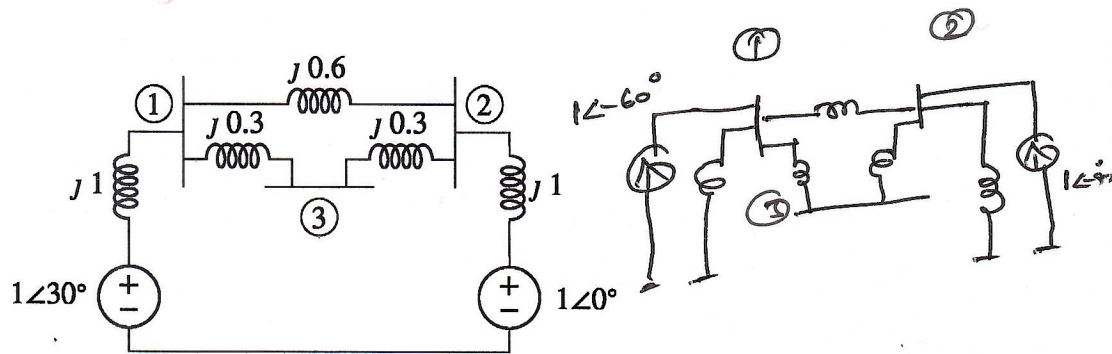5. Consider the reactance network shown here.



(a) Find the voltage at node 3.

(b) Find the voltage at node 3 after connecting a capacitor having a reactance of 2.0 per unit connected between node 3 to the reference node. (Hint : Use Thevenin equivalent.)

a)

$$Y_{bus} = \begin{bmatrix} -j6 & j1.67 & j3.33 \\ j1.67 & -j6 & j3.33 \\ j3.33 & j3.33 & -j6.67 \end{bmatrix}$$

$$Z_{bus} = Y_{bus}^{-1} = \begin{bmatrix} j0.57 & j0.43 & j0.5 \\ j0.43 & j0.57 & j0.5 \\ j0.5 & j0.5 & j0.65 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = [Y_{bus}]^{-1} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} V_3 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0.933 + j0.25 \\ 0.966 \angle 15^\circ \end{bmatrix}$$

b) By Thevenin method:

$$V_3^{new} = V_{Th} \times \frac{-j2}{Z_{Th} - j2}$$

$$= 0.966 \angle 15^\circ \times \frac{-j2}{j0.65 - j2}$$

$$V_3^{new} = 1.38 + j0.37$$

$$V_3^{new} = 1.43 \angle 15^\circ$$

By Y_{bus} modification:

$$Y_{33} = -j6.67 + \frac{1}{-j2} = -j6.17$$

$$Z_{bus} = \begin{bmatrix} -j6 & j1.67 & j3.33 \\ j1.67 & -j6 & j3.33 \\ j3.33 & j3.33 & -j6.17 \end{bmatrix}$$

$$V_3^{new} = Z_{bus}^{-1} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} j0.74 \\ j0.74 \\ j0.96 \end{bmatrix}$$

$$= 1.37 + j0.37$$

$$V_3^{new} = 1.42 \angle 15^\circ$$