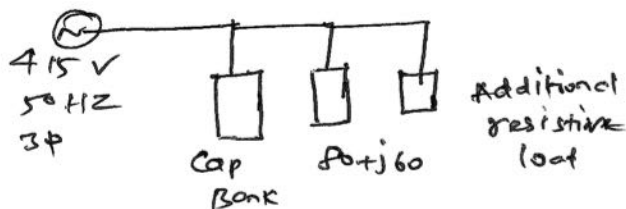



There are 5 problems. They carry equal marks.

$$(5 \times 2 = 10)$$

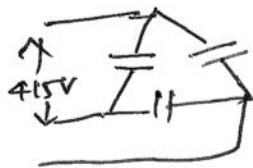1. A three-phase cable is supplying 80 kW and 60 kVAR to an inductive load. It is intended to supply an additional resistive load through the same cable without increasing the heat dissipation in the cable, by providing a three-phase bank of capacitors connected in delta across the load. Given the line voltage is 415 V, 50 Hz, and the capacitance per phase of the bank is $200 \mu\text{F}$, find the additional resistive load in kW which can be supplied.



To have the same heat dissipation, the apparent power (KVA) of the total loads must be the same.




$$\begin{aligned} Q_c &= 3 \times 415^2 \times \omega \times 200 \times 10^{-6} \\ (3\phi) &= 32.5 \text{ KVAR} \end{aligned}$$

$$\begin{aligned} S &= 100 \text{ KVA} \\ S^2 &= (80 + P_{\text{add}})^2 + (60 - 32.5)^2 \end{aligned}$$

$$\therefore P_{\text{add}} = 16.13 \text{ kW}$$

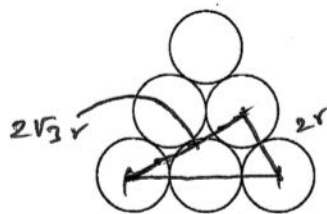2. Determine the geometric mean radius (GMR) of the following configurations for inductance in terms of the radius r of the individual strand.



$$\begin{aligned} GMR_L &= \sqrt[3]{(0.7788r \times 2r \times 4r \times 2\sqrt{3}r \times 2r \times 4r) \times 36 (0.7788r \times 2r \times 2r \times 2r \times 2r \times 2\sqrt{3}r)^3} \\ &= (0.7788)^{1/6} \times r \times 2 \times (2)^{1/2} \end{aligned}$$

$$GMR_L = 2.1024 r$$

3. For a 400 km long transmission line, the series impedance is $(0 + j0.5) \Omega/\text{km}$ and the shunt admittance is $(0 + j5) \mu\text{S}/\text{km}$. The magnitude of the series impedance (in Ω) of the equivalent- π circuit of the transmission line is

$$Z' = Z_c \sinh \gamma l \quad (\text{Equivalent } \pi\text{-model})$$


$$Z_c = \sqrt{\frac{z}{y}} = \sqrt{\frac{j0.5}{j5 \times 10^{-6}}} = 316.22 \Omega$$

$$\gamma = \sqrt{zy} = \sqrt{j0.5 \times 5 \times 10^{-6}} = j0.0016 \text{ rad/km}$$

$$Z' = 316.22 \times \sinh(j0.0016 \times 400)$$

$$Z' = j186.93 \Omega \quad \boxed{|Z| \approx 187 \Omega}$$

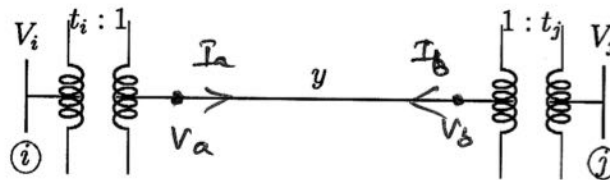4. Two buses, i and j are connected with a transmission line of admittance Y , at the two ends of which there are ideal transformers with turns ratios as shown below.



Find the bus admittance matrix.

$$V_a = \frac{V_i}{t_i}, \quad V_b = \frac{V_j}{t_j}, \quad I_a = I_i t_i, \quad I_b = I_j t_j$$

$$I_a = (V_a - V_b)Y = \frac{V_i}{t_i}Y - \frac{V_j}{t_j}Y$$

$$I_b = (V_b - V_a)Y = \frac{V_j}{t_j}Y - \frac{V_i}{t_i}Y$$

$$I_i = \frac{I_a}{t_i} = \frac{V_i}{t_i^2}Y - \frac{V_j}{t_i t_j}Y \quad \text{--- (1)}$$

$$I_j = \frac{I_b}{t_j} = -\frac{V_i}{t_i t_j}Y + \frac{V_j}{t_j^2}Y \quad \text{--- (2)}$$

From (1) and (2)

$$\begin{bmatrix} I_i \\ I_j \end{bmatrix} = \begin{bmatrix} \frac{Y}{t_i^2} & -\frac{Y}{t_i t_j} \\ -\frac{Y}{t_i t_j} & \frac{Y}{t_j^2} \end{bmatrix} \begin{bmatrix} V_i \\ V_j \end{bmatrix}$$

Y_{Bus}

5. Bus 1 with voltage magnitude $V_1 = 1$ p.u. is sending reactive power Q_{12} to bus 2 with voltage magnitude $V_2 = 0.9$ p.u. through a lossless transmission line of reactance X . Keeping V_2 at 0.9 p.u., V_1 is changed so that Q_{12} is increased by 10%. Real power flow under both the conditions is zero. What is the new V_1 in p.u.?

$$Q_{12} = \frac{V_1^2}{X} - \frac{V_1 V_2 \cos(\delta_1 - \delta_2)}{X}$$

Since $P_{12} = 0$, $\delta_1 - \delta_2 = 0$

$$\therefore Q_{12} = \frac{1 \times 0.1}{X} = \frac{0.1}{X}$$

$$Q_{12_{\text{new}}} = 1.1 \times Q_{12(\text{old})}$$

$$Q_{12_{\text{new}}} = \frac{1.1 \times 0.1}{X}$$

$$\frac{1.1 \times 0.1}{X} = \frac{V_1^2}{X} - \frac{V_1 \times 0.9}{X}$$

Solving then $V_1 = 1.01, -0.11$

Picking the feasible solution

$$\boxed{V_1 = 1.01 \text{ p.u.}}$$