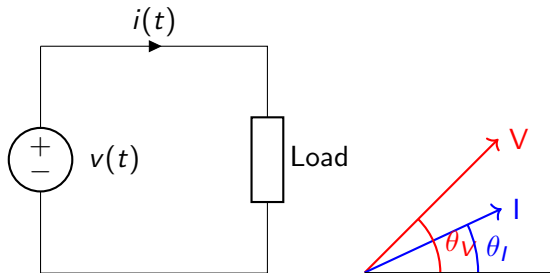


Power in Single Phase AC Circuits

Let us consider the following circuit.



Let

$$v(t) = V_m \sin(\omega t + \theta_V) = \sqrt{2}V \sin(\omega t + \theta_V)$$

$$i(t) = I_m \sin(\omega t + \theta_I) = \sqrt{2}I \sin(\omega t + \theta_I)$$

The **instantaneous power** delivered to the load is

$$p(t) = v(t)i(t)$$

$$p(t) = V_m \sin(\omega t + \theta_V) I_m \sin(\omega t + \theta_I)$$

$$p(t) = \frac{V_m I_m}{2} (\cos(\theta_V - \theta_I) - \cos(2\omega t + \theta_V + \theta_I))$$

$$p(t) = \frac{V_m I_m}{2} \cos(\theta_V - \theta_I) - \frac{V_m I_m}{2} \cos(2\omega t + \theta_V + \theta_I)$$

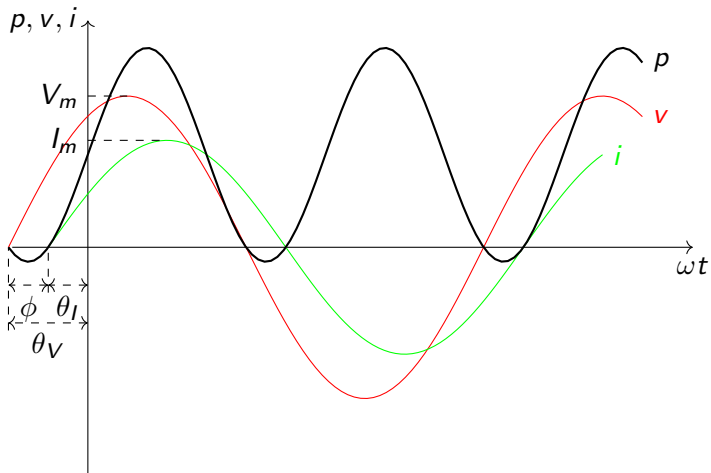


Figure: Voltage, current and power in RL circuit

Let $\theta_V - \theta_I$ be ϕ .

$$p(t) = VI \cos \phi - VI \cos(2\omega t + \theta_V + \theta_I)$$

$$p(t) = VI \cos \phi - VI \cos(2\omega t + \theta_V - \theta_I + 2\theta_I)$$

$$p(t) = VI \cos \phi - VI \cos(2\omega t + 2\theta_I + \phi)$$

$$p(t) = \underbrace{VI \cos \phi (1 - \cos(2\omega t + 2\theta_I))}_{p_I} + \underbrace{VI \sin \phi \sin(2\omega t + 2\theta_I)}_{p_{II}}$$

p_I has an average value of $VI \cos \phi$ which is called the **average power**.

p_{II} does not have an average. But its maximum value is $VI \sin \phi$ which is called **reactive power**.

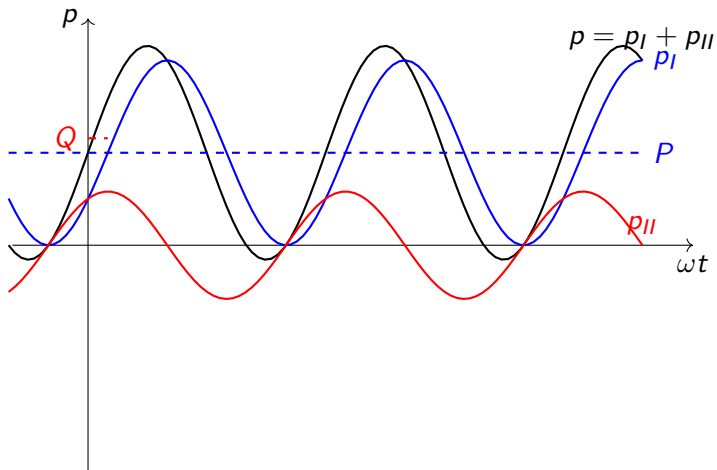


Figure: Power in RL circuit

Power

The average power P is

$$P = \frac{V_m I_m}{2} \cos(\theta_V - \theta_I) = VI \cos(\phi)$$

where $\phi = \theta_V - \theta_I$. Its unit is watts (W).

The reactive power Q is

$$Q = VI \sin \phi \quad \text{VAr}$$

The apparent power S is

$$|S| = VI$$

Its unit is **volt-ampere (VA)**.

The ratio of real power (P) to apparent power is called as the **power factor (pf)**.

$$\text{pf} = \frac{VI \cos \phi}{VI} = \cos \phi$$

Since $\cos \phi$ can never be greater than unity, $P < |S|$.

Complex Power

Let us define voltage phasor and current phasor.

$$\mathbf{V} = V\angle\theta_V, \quad \mathbf{I} = I\angle\theta_I$$

The complex power \mathbf{S} is

$$\mathbf{S} = \mathbf{V}\mathbf{I}^*$$

$$\mathbf{S} = V\angle\theta_V I\angle -\theta_I$$

$$= VI\angle(\theta_V - \theta_I)$$

$$\mathbf{S} = VI \cos \phi + jVI \sin \phi$$

The real part of \mathbf{S} is called the average power (P). The imaginary part of \mathbf{S} is called the reactive power (Q).

$$\mathbf{S} = P + jQ$$

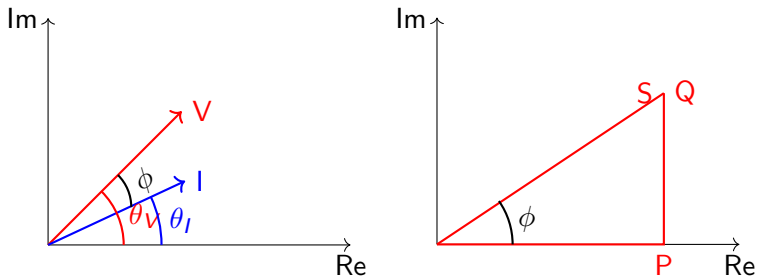


Figure: RL load

If V leads I ($\phi > 0$), power factor is lagging.

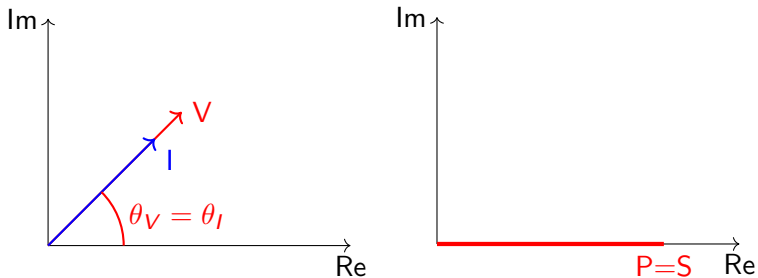


Figure: Resistive Load

If V and I are in phase ($\phi = 0$), power factor is unity.


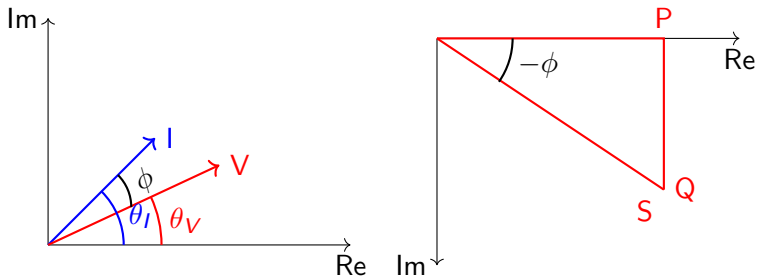


Figure: RC load

If I leads V ($\phi < 0$), power factor is leading.

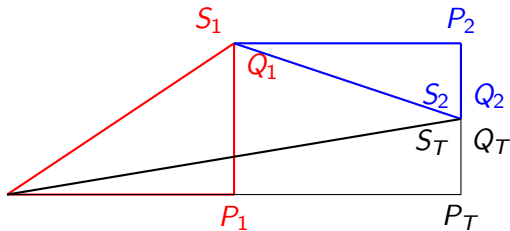For two loads (inductive and capacitive) in parallel,





$$P_T = P_1 + P_2; \quad Q_T = Q_1 + Q_2$$

But

$$|S_T| \neq |S_1| + |S_2|$$

Power Factor Control

- If pf decreases, the current will increase to supply the same real power.
- This will increase the line loss. (It is an additional cost to a utility.)
- Capacitors which supply reactive power are connected in parallel to improve the power factor.

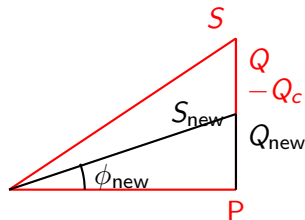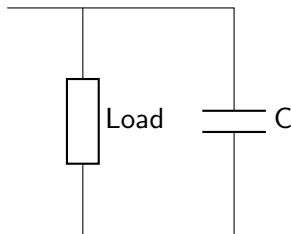


Example 1 : A single-phase inductive load draws 1 kW at 0.6 power-factor lagging from a 230 V AC supply.

- 1 Find the current it draws.
- 2 Find the value of a capacitor to be connected in parallel with the load to raise the power factor to 0.9 lagging. Determine the current under this condition.

1

$$I = \frac{1000}{230 \times 0.6} = 7.24 \text{ A}$$
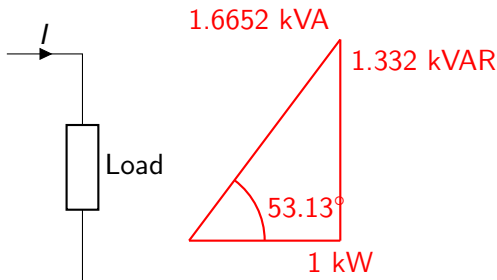
$$Q = 230 \times 7.24 \times 0.8 = 1.332 \text{ kVAR}$$



$$pf_{\text{new}} = 0.9; \quad \phi_{\text{new}} = 25.84^\circ$$

$$Q_{\text{new}} = Q_L - Q_c$$


$$Q_{\text{new}} = P \times \tan 25.84^\circ = 484.32 \text{ VAr}$$

$$Q_c = 847.68 \text{ VAr}$$

$$Q_c = V^2 \omega C$$

$$C = 51 \mu F$$
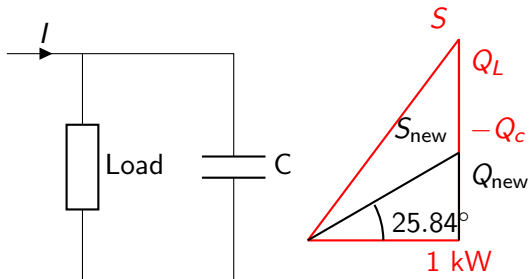
$$I = \frac{1000}{230 \times 0.9} = 4.83 \text{ A}$$



Power in Balanced Three Phase Circuits

Let v_a , v_b and v_c be the instantaneous voltages of a balanced three phase source.

$$\begin{aligned}v_a &= \sqrt{2}V \sin(\omega t + \theta_V) \\v_b &= \sqrt{2}V \sin(\omega t + \theta_V - 120^\circ) \\v_c &= \sqrt{2}V \sin(\omega t + \theta_V - 240^\circ)\end{aligned}$$

When it supplies a balanced load,

$$\begin{aligned}i_a &= \sqrt{2}I \sin(\omega t + \theta_I) \\i_b &= \sqrt{2}I \sin(\omega t + \theta_I - 120^\circ) \\i_c &= \sqrt{2}I \sin(\omega t + \theta_I - 240^\circ)\end{aligned}$$

The instantaneous power is

$$p = v_a i_a + v_b i_b + v_c i_c$$

$$\begin{aligned} p &= \sqrt{2}V_p \sin(\omega t + \theta_V) \times \sqrt{2}I_p \sin(\omega t + \theta_I) \\ &\quad \sqrt{2}V_p \sin(\omega t + \theta_V - 120^\circ) \times \sqrt{2}I_p \sin(\omega t + \theta_I - 120^\circ) \\ &\quad \sqrt{2}V_p \sin(\omega t + \theta_V - 240^\circ) \times \sqrt{2}I_p \sin(\omega t + \theta_I - 240^\circ) \\ p &= V_p I_p \cos(\theta_V - \theta_I) + V_p I_p \cos(2\omega t + \theta_V + \theta_I) \\ &\quad V_p I_p \cos(\theta_V - \theta_I) + V_p I_p \cos(2\omega t + \theta_V + \theta_I - 120^\circ) \\ &\quad V_p I_p \cos(\theta_V - \theta_I) + V_p I_p \cos(2\omega t + \theta_V + \theta_I - 240^\circ) \end{aligned}$$

$$p = 3V_p I_p \cos \phi$$

where $\phi = \theta_V - \theta_I$.

The instantaneous power in a 3 phase balanced system is constant.

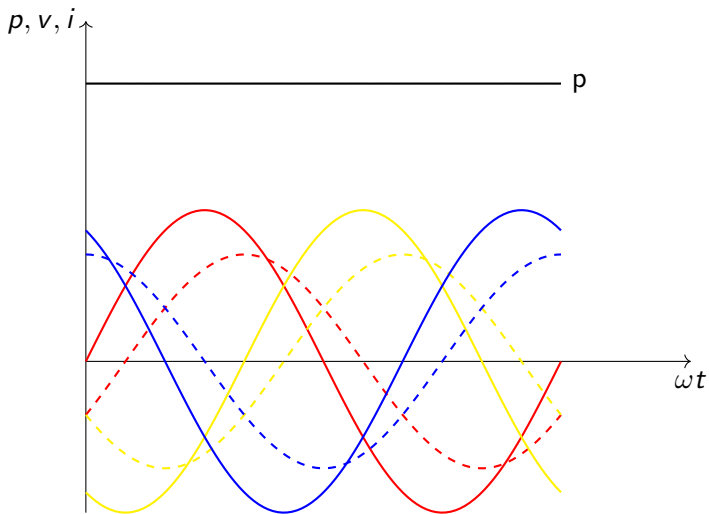


Figure: Voltage, current and power in a R-L load

The average/real power in a 3-phase system is

$$P = 3V_p I_p \cos \phi \quad \text{Watts}$$

In a Y connected load, $V_L = \sqrt{3}V_p$ and $I_L = I_p$,

$$P = \sqrt{3}V_L I_L \cos \phi$$

In a Δ connected load, $V_L = V_p$ and $I_L = \sqrt{3}I_p$,

$$P = \sqrt{3}V_L I_L \cos \phi$$

Therefore, the three phase real power is

$$P = 3V_p I_p \cos \phi = \sqrt{3}V_L I_L \cos \phi$$

Since the instantaneous power in a 3-phase balanced system is constant, it does not mean that there is no reactive power. Still the instantaneous power of individual phases is pulsating.

The 3-phase reactive power is

$$Q = 3V_p I_p \sin \phi = \sqrt{3} V_L I_L \sin \phi \quad \text{VAR}$$

The apparent power is

$$|S| = \sqrt{P^2 + Q^2} = 3V_p I_p = \sqrt{3} V_L I_L \quad \text{VA}$$

Per Phase Analysis


If a three phase system is balanced and there is no mutual inductance between phases, it is enough to analyze it on per phase basis.

- 1 Convert all Δ connected sources and loads into equivalent Y connections.
- 2 Solve for phase a variables using the phase a circuit with neutrals connected.
- 3 Other phase variables can be found from the phase a variables using the symmetry.
- 4 If necessary, find line-line variables from the original circuit.

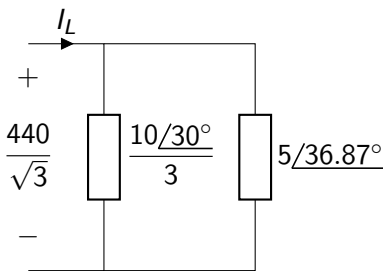Example 2: Consider a system where a three phase 440 V, 50 Hz source is supplying power to two loads. Load 1 is a Δ connected load with a phase impedance of $10\angle 30^\circ \Omega$ and load 2 is a Y connected load with a phase impedance of $5\angle 36.87^\circ \Omega$.

- 1 Find the line current and the overall power factor of the system.
- 2 Determine the capacitance per phase in μF of a three phase bank of delta connected capacitors to be added in parallel to the load to improve the overall power factor unity. Find the line current under this condition.

- ① The per phase equivalent circuit after using Δ to Y transformation,




$$I_L = \frac{440/\sqrt{3}}{10/3/30^\circ} + \frac{440/\sqrt{3}}{5/36.87^\circ}$$

$$I_L = 106.64 - j68.6 \text{ A}$$

$$I_L = 126.8/\underline{-32.75^\circ} \text{ A}$$

$$pf = \cos(-32.75^\circ) = 0.84 \text{ lag}$$

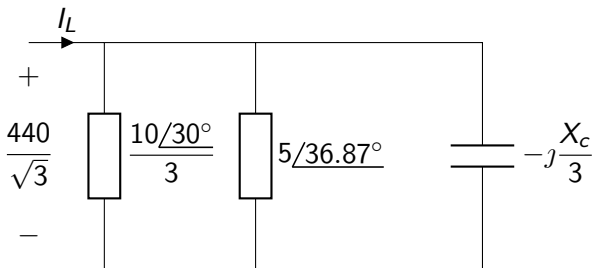- 2 The per phase equivalent circuit with a capacitor bank



To make overall power factor unity, I_L must be in phase with the voltage.

$$\therefore I_c = j68.6\text{A}$$

$$X_c = \frac{3 \times 440}{\sqrt{3} \times 68.6} = 11.11 \Omega$$

$$C = 286.52 \mu\text{F}$$

Example 3: Consider a system where a three phase 400 V, 50 Hz source is supplying power to two loads. Load 1 draws 5 kW at 0.8 pf lagging and load 2 draws 5 kW at unity power factor. The voltage across the loads is 400 V.

- 1 Find the line current and the overall power factor.
- 2 Find the value of kVAR required from a bank of capacitors connected across the loads to improve the overall power factor to unity. Determine the line current under this condition.

1

$$I_{L1} = \frac{5000}{\sqrt{3} \times 400 \times 0.8} = 9 \text{ A}$$

$$I_{L2} = \frac{5000}{\sqrt{3} \times 400 \times 1} = 7.2; \text{ A}$$

$$I_L = 9 \angle -36.87^\circ + 7.2 \angle 0^\circ = 15.38 \angle -20.56^\circ \text{ A}$$

$$pf = 0.9363 \text{ lag}$$

$$Q_T = Q_1 + Q_2 = 3.75 + 0 = 3.75 \text{ kVAR}$$

- ② To make overall power factor unity,

$$Q_C + Q_T = 0$$

$$Q_C = -3.75 \text{ kVAR}$$

(-ve indicates that the capacitor supplies reactive power.)

$$\therefore Q_C = 3.75 \text{ kVAR}$$

When pf is unity, $S = P$.

$$I_L = \frac{P_T}{\sqrt{3}V_L} = \frac{10 \times 10^3}{\sqrt{3} \times 400} = 14.4 \text{ A}$$

$$I_L = 14.4/\underline{0^\circ} \text{ A}$$